

Description: In this project, I will build a bomb using a state machine, a down counter, and lights on the fpga.


First we need to create a down counter:

```

1 // Implements a 4 bits down counter 9 down to 0 with several enable inputs and loadN data.
2 // It outputs count and asynchronous terminal count, tc, signal
3 module down_counter
4 (
5     input logic clk,
6     input logic resetN,
7     input logic loadN,
8     input logic enable1,
9     input logic enable2,
10    input logic enable3,
11    input logic [3:0] datain,
12
13    output logic [3:0] count,
14    output logic tc
15 );
16
17 // Down counter
18 always_ff @(posedge clk or negedge resetN)
19 begin
20
21     if (!resetN) begin // Asynchronous reset
22         count <= 4'h0;
23     end
24     else begin // Synchronic logic
25         //-----
26         if (!loadN) begin
27             count <= datain;
28         end else if (enable1 && enable2 && enable3) begin
29             if (count == 4'b0000) begin
30                 count <= 4'b1001; // Reset to 9 when count reaches 0
31             end else begin
32                 count <= count - 1; // Decrement counter
33             end
34         end
35         //-----
36     end //synch
37 end //always
38 // Asynchronous tc
39
40 assign tc = (count == 0) ? 1'b1 : 1'b0;
41 //-----
42
43 endmodule

```

Check with waveform:

 


Next step is to design a down counter with 2 digits:

```

4 module bcddn
5 (
6     input logic clk,
7     input logic resetN,
8     input logic loadN,
9     input logic enable1,
10    input logic enable2,
11
12    output logic [3:0] countL,
13    output logic [3:0] countH,
14    output logic tc
15 );
16 // Parameters defined as external, here with a default value - to be updated
17 // in the upper hierarchy file with the actual bomb down counting values
18 //
19 parameter logic [3:0] datainL = 4'h2 ;
20 parameter logic [3:0] datainH = 4'h1 ;
21 //
22 logic tcLow, tcHigh; // internal variables terminal count
23 // Low counter instantiation
24 down_counter lowc(.clk(clk),
25                  .resetN(resetN),
26                  .loadN(loadN),
27                  .enable1(enable1),
28                  .enable2(enable2),
29                  .enable3(1'b1),
30                  .datain(datainL),
31                  .count(countL),
32                  .tc(tcLow));
33 // High counter instantiation
34 down_counter highc(.clk(clk),
35                  .resetN(resetN),
36                  .loadN(loadN),
37                  .enable1(enable1),
38                  .enable2(enable2),
39                  .enable3(tcLow),
40                  .datain(datainH),
41                  .count(countH),
42                  .tc(tcHigh));
43 //
44 assign tc = (countH == 0 && countL == 0) ? 1'b1 : 1'b0; // ## initializing a variable, to enable compilation, change if needed
45 //
46 endmodule


```

Check with waveform:

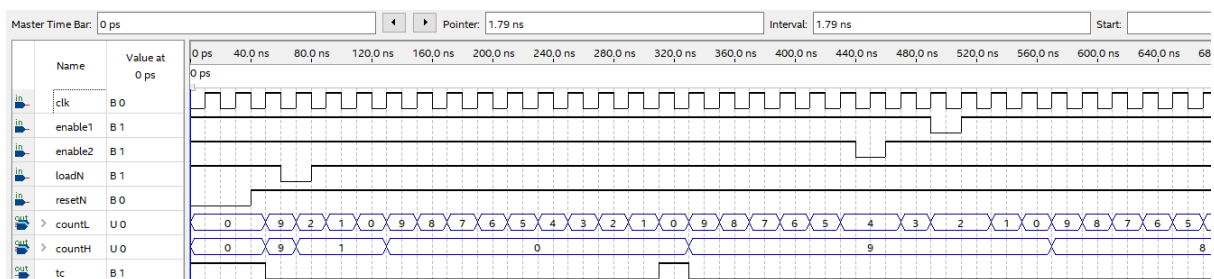

The next step is to create a traffic light, which will allow us to use the light on the bomb as a signal before the explosion.

The FSM:

 

The code:

```
module ramzor
(
    input logic clk, // 50 MHz clock
    input logic resetN,
    input logic switchN, // pedestrian switch to change the light

    output logic redLight, // output to the red lamp
    output logic yellowLight, // output to the yellow lamp
    output logic greenLight // output to the green lamp '
);

//-----
// localparam SIMULATION_MODE_ON = 0 ; // Run Mode : unmask the line for real run
// localparam SIMULATION_MODE_ON = 1 ; // simulation mode : unmask the line for
simulation run
//-----
// state machine and parameters declaration
enum logic [1:0] {s_red, s_red_yellow, s_green, s_yellow} SMramzor; // state
machine
    logic [3:0] counter; // count down second timer

    logic t_sec; // A short pulse, once every second.
    assign timerEnded = (counter == 4'b0) ;

//-----

    localparam logic [3:0] RED_OR_GREEN_TIME = 'd5;
    localparam logic [3:0] YELLOW_TIME = 'd1;

    localparam logic LED_ON = 1'b1;
    localparam logic LED_OFF = 1'b0;

//-----
// Instance of 1Hz sub module as a time counter for the state machine

one_sec_counter #(SIMULATION_MODE(SIMULATION_MODE_ON)) one_sec_counter
(.clk(clk),
                                .resetN(resetN),
                                .turbo(0),
                                .one_sec(t_sec) );
```

```

//-----

//hexss
//-----

// synchronous code, executed once every clock to update the current state and outputs

always_ff @(posedge clk or negedge resetN) // State machine logic ////
begin

    if ( !resetN ) begin // Asynchronous reset, initialize the state machine
        SMramzor <= s_red;
        counter <= RED_OR_GREEN_TIME;
        redLight <= 1'b1 ;
        yellowLight <= 1'b0 ;
        greenLight <= 1'b0 ;

        end // asynch
    else begin // Synchronic logic of the state machine; once
every clock

//-----
        if ( t_sec ) begin // perform once every timer pulse ( every 0.1 sec )

            if ( !timerEnded ) // timer didn't finish
                counter <= counter - 4'b1; // decremnt the counter

            end

//-----
        // state machine

        // default outputs
        redLight <= 1'b0 ;
        yellowLight <= 1'b0 ;
        greenLight <= 1'b0 ;

        case ( SMramzor )

//Note: the implementation of the red Yellow
state is already given you as an example

        //      =====
        //      =====
        s_red_yellow: begin

            redLight <= 1'b1 ;

```

```

        yellowLight <= 1'b1 ;

        if ( timerEnded ) // timer finished
            begin
                SMramzor <= s_green;

//next state is green
                counter <=
RED_OR_GREEN_TIME; // reload counter with the next value.
            end // if

        end // s_red_yellow

//-----
s_green: begin
    greenLight <= 1'b1;
    if ( timerEnded )
        begin
            SMramzor <= s_yellow; // next state
            counter <= YELLOW_TIME; //
            the timer now is 1sec
        end
    end


//-----
s_yellow: begin
    yellowLight <= 1'b1;
    if ( timerEnded )
        begin
            SMramzor <= s_red; // next state is
            red
            counter <=
RED_OR_GREEN_TIME; // the timer now is 5sec
        end
    end

//-----
s_red: begin
    redLight <= 1'b1;
    if (!switchN) begin
        SMramzor <= s_red_yellow; // next state is
        yellow
        counter <= YELLOW_TIME; // the timer
        now is 1sec
    end
    else if (timerEnded)
        begin
            SMramzor <= s_red_yellow; // next
            state is yellow


```

```
//-----  
counter <= YELLOW_TIME; //  
the timer now is 1sec  
  
end  
end  
  
//===== default : begin  
// ===== SMramzor <= s_red; //next state  
end // default  
  
endcase  
end // if reset  
  
end // always_ff state machine ///////////////////////////////////  
  
endmodule  
  
// end code here
```

**Bomb Diagram State:**

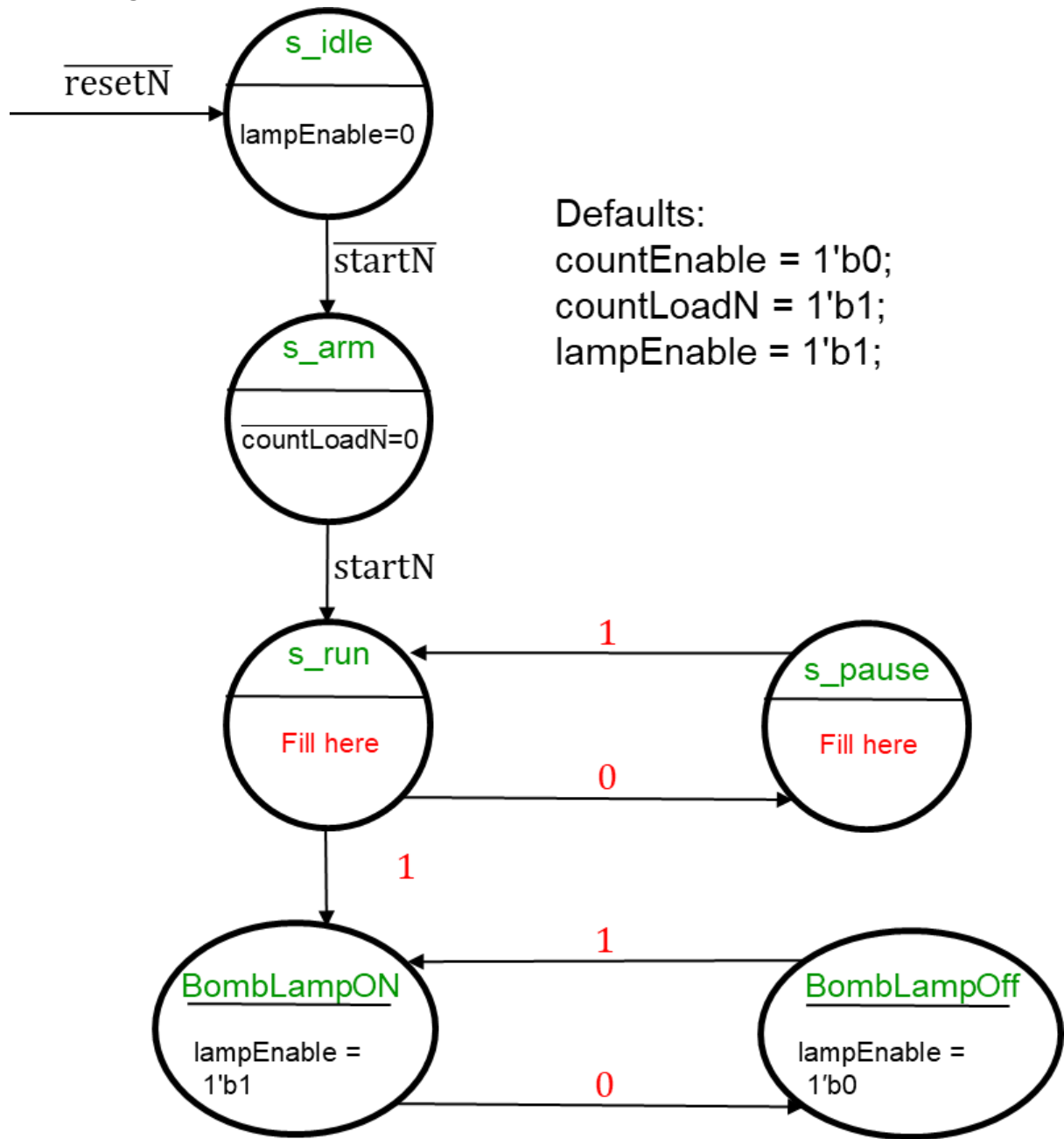

## Block Diagram:

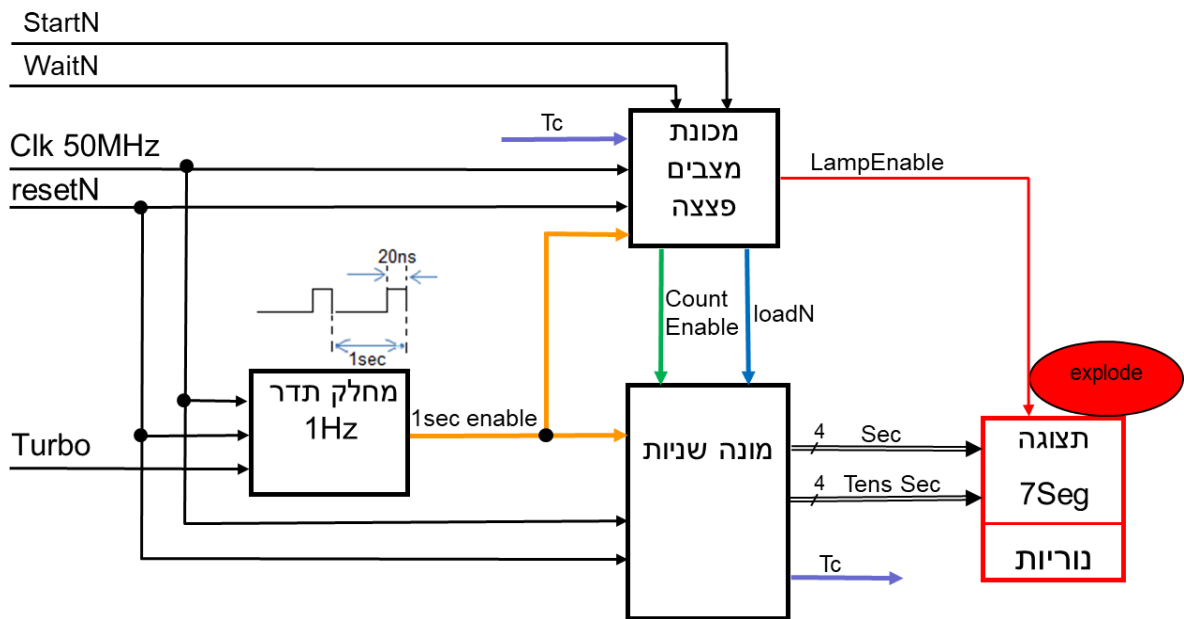

## Bomb Verilog Code:

// Implements the state machine of the bomb mini-project

module bomb

```
(
    input logic clk,
    input logic resetN,
    input logic startN,
    input logic waitN,
    input logic OneSecPulse,
    input logic timerEnd,
```

```
    output logic countLoadN,
    output logic countEnable,
    output logic lampEnable
```

```
);
```

//-----

// state machine declaration

```
enum logic [2:0] {s_idle, s_arm, s_run, s_pause, s_lampOff, s_lampOn} SMbomb;
```

//-----

// synchronous code: executed once every clock to update the current state

```
always @(posedge clk or negedge resetN)
```

```
begin
```

```
    if ( !resetN ) begin // Asynchronous reset
```



```

        SMBomb <= s_idle;
        countEnable <= 1'b0;
        countLoadN <= 1'b1;
        lampEnable <= 1'b0;

    end

else          // Synchronic logic FSM
    begin
        // default outputs
        countEnable <= 1'b0;
        countLoadN <= 1'b1;
        lampEnable <= 1'b1;

        case (SMBomb) // logically defining what is the next state, and the output

// =====
            s_idle: begin
// =====
                if (startN == 1'b0)
                    SMBomb <= s_arm;
                end // idle

//-----
s_arm: begin
    countLoadN <= 1'b0; // Load countdown timer
    if (startN) begin // Wait for startN to be released
        SMBomb <= s_run;
        countEnable <= 1'b1; // Start countdown
    end else begin
        SMBomb <= s_arm;
    end
end

s_run: begin
    countEnable <= 1'b1; // Continue countdown
    if (!waitN) begin
        SMBomb <= s_pause;
        countEnable <= 1'b0; // Pause countdown
    end else if (timerEnd) begin
        SMBomb <= s_lampOff; // Timer ended
    end else begin
        SMBomb <= s_run;
    end
end

s_pause: begin

```

```

countEnable <= 1'b0; // Countdown is paused
if (waitN) begin // Wait for waitN to be released
    SMBomb <= s_run;
    countEnable <= 1'b1; // Resume countdown
end else begin
    SMBomb <= s_pause;
end
end
end

```

```

s_lampOff: begin
    lampEnable <= 1'b0; // Turn off lamp
    if (OneSecPulse) begin // Blink display
        SMBomb <= s_lampOn;
    end else begin
        SMBomb <= s_lampOff;
    end
end
end

```

```

s_lampOn: begin
    lampEnable <= 1'b1; // Turn on lamp
    if (OneSecPulse) begin // Continue blinking
        SMBomb <= s_lampOff;
    end else begin
        SMBomb <= s_lampOn;
    end
end
end

```

```

//-----
//          =====
//          default : begin
//          =====
//                      SMBomb <= s_idle;
//                      end // default

        endcase
    end //else

    end // always sync



    // outputs logic

endmodule


// end code here

```


## Waveform Simulation:

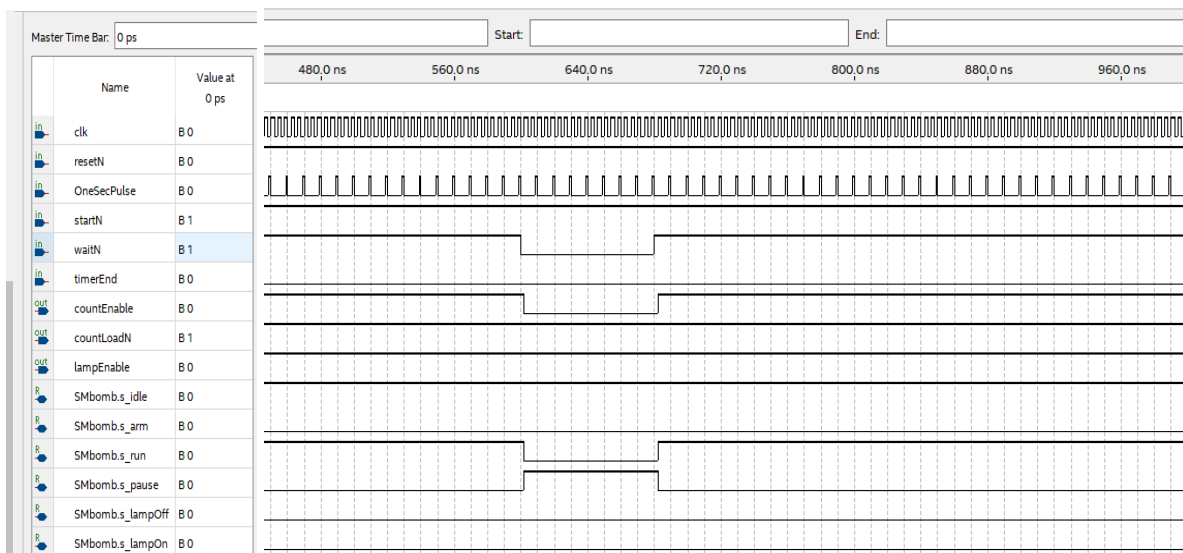 

## Quartus FSM For The Design:

 

## Top Hierarchy For The Project:

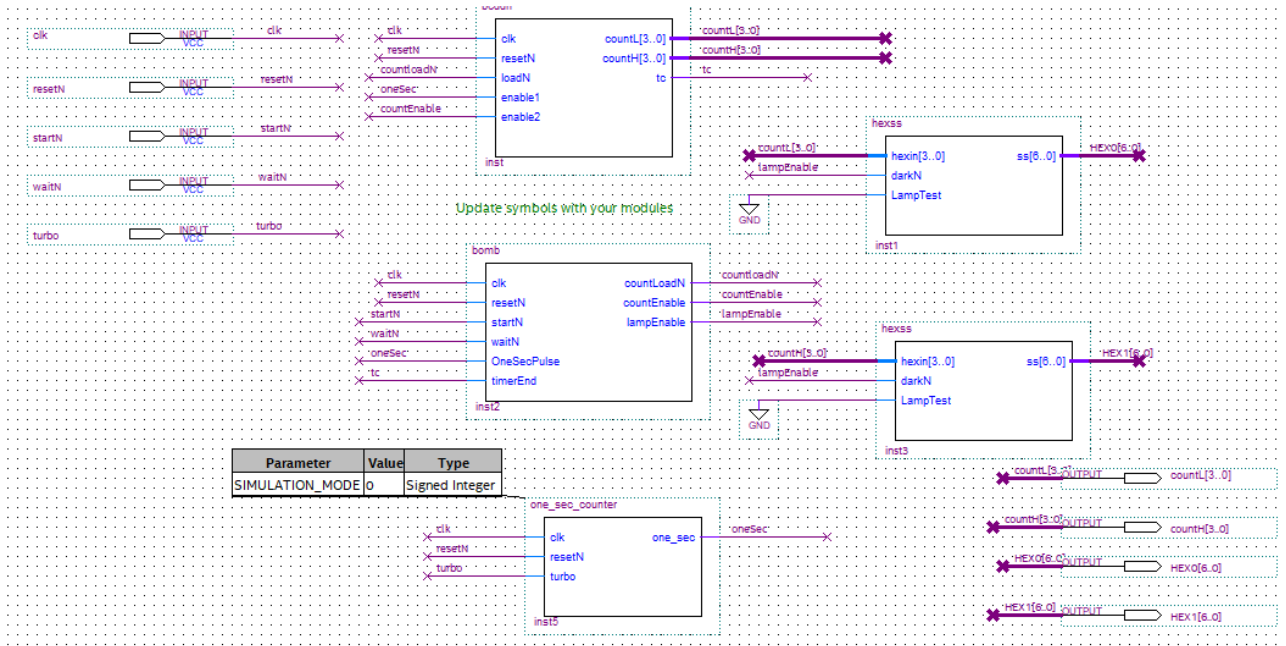

## Compilation on the FPGA:

Node Name	Direction	Location	I/O Bank	VREF Group	Fitter Location	I/O Standard	Reserved	Current Strength	Slew Rate
in startN	Input	PIN_AA14	3B	B3B_N0	PIN_AA14	3.3-V LVTTTL		16mA (default)	
in waitN	Input	PIN_AA15	3B	B3B_N0	PIN_AA15	3.3-V LVTTTL		16mA (default)	
in turbo	Input	PIN_AB30	5B	B5B_N0	PIN_AB30	3.3-V LVTTTL		16mA (default)	
in clk	Input	PIN_AF14	3B	B3B_N0	PIN_AF14	3.3-V LVTTTL		16mA (default)	
in resetN	Input	PIN_AJ4	3B	B3B_N0	PIN_AJ4	3.3-V LVTTTL		16mA (default)	
out countH[3]	Output	PIN_AB22	5A	B5A_N0	PIN_AB22	3.3-V LVTTTL		16mA (default)	1 (default)
out countL[0]	Output	PIN_AB23	5A	B5A_N0	PIN_AB23	3.3-V LVTTTL		16mA (default)	1 (default)
out countL[1]	Output	PIN_AC23	4A	B4A_N0	PIN_AC23	3.3-V LVTTTL		16mA (default)	1 (default)
out HEX1[3]	Output	PIN_AD17	4A	B4A_N0	PIN_AD17	3.3-V LVTTTL		16mA (default)	1 (default)
out countL[2]	Output	PIN_AD24	4A	B4A_N0	PIN_AD24	3.3-V LVTTTL		16mA (default)	1 (default)
out HEX1[2]	Output	PIN_AE16	4A	B4A_N0	PIN_AE16	3.3-V LVTTTL		16mA (default)	1 (default)
out HEX1[5]	Output	PIN_AE17	4A	B4A_N0	PIN_AE17	3.3-V LVTTTL		16mA (default)	1 (default)
out HEX1[4]	Output	PIN_AE18	4A	B4A_N0	PIN_AE18	3.3-V LVTTTL		16mA (default)	1 (default)
out countH[1]	Output	PIN_AE24	4A	B4A_N0	PIN_AE24	3.3-V LVTTTL		16mA (default)	1 (default)
out HEX1[0]	Output	PIN_AF16	4A	B4A_N0	PIN_AF16	3.3-V LVTTTL		16mA (default)	1 (default)
out countH[2]	Output	PIN_AF24	4A	B4A_N0	PIN_AF24	3.3-V LVTTTL		16mA (default)	1 (default)
out countH[0]	Output	PIN_AF25	4A	B4A_N0	PIN_AF25	3.3-V LVTTTL		16mA (default)	1 (default)
out HEX0[3]	Output	PIN_AG16	4A	B4A_N0	PIN_AG16	3.3-V LVTTTL		16mA (default)	1 (default)
out HEX0[2]	Output	PIN_AG17	4A	B4A_N0	PIN_AG17	3.3-V LVTTTL		16mA (default)	1 (default)
out HEX0[5]	Output	PIN_AG18	4A	B4A_N0	PIN_AG18	3.3-V LVTTTL		16mA (default)	1 (default)
out countL[3]	Output	PIN_AG25	4A	B4A_N0	PIN_AG25	3.3-V LVTTTL		16mA (default)	1 (default)
out HEX0[4]	Output	PIN_AH17	4A	B4A_N0	PIN_AH17	3.3-V LVTTTL		16mA (default)	1 (default)
out HEX0[6]	Output	PIN_AH18	4A	B4A_N0	PIN_AH18	3.3-V LVTTTL		16mA (default)	1 (default)
out HEX1[1]	Output	PIN_V16	4A	B4A_N0	PIN_V16	3.3-V LVTTTL		16mA (default)	1 (default)
out HEX1[6]	Output	PIN_V17	4A	B4A_N0	PIN_V17	3.3-V LVTTTL		16mA (default)	1 (default)
out HEX0[1]	Output	PIN_V18	4A	B4A_N0	PIN_V18	3.3-V LVTTTL		16mA (default)	1 (default)
out HEX0[0]	Output	PIN_W17	4A	B4A_N0	PIN_W17	3.3-V LVTTTL		16mA (default)	1 (default)